

Component	Pico Pin	Function
Button A	GP14	Input A
Button B	GP15	Input B
Button C	GP16	Input C
LED F	GP13	Output
GND	GND	Ground
3.3V	3.3V	Pull-up Supply

Pico Pin Mapping for F Output Circuit

Component	Arduino Pin	Function
Button A	D2	Input A
Button B	D3	Input B
Button C	D4	Input C
LED F	D5	Output
GND	GND	Ground
5V	VCC	Pull-up Supply

Arduino Pin Mapping

3. Write logic in Python:

$$F = \overline{(A + B) + (A + C)} + C$$

4. Toggle buttons and test LED output.

For Arduino:

1. Open Arduino IDE.
2. Use `digitalRead()` to read A, B, C.
3. Implement logic for F.
4. Output to `digitalWrite(pin, F)`.
5. Upload and observe result on LED.


Conclusion

The logic circuit is analyzed and verified with the combination:

$$A = 0, B = 1, C = 0 \Rightarrow F = 1$$

Implemented using both theoretical truth table and GPIO hardware logic.

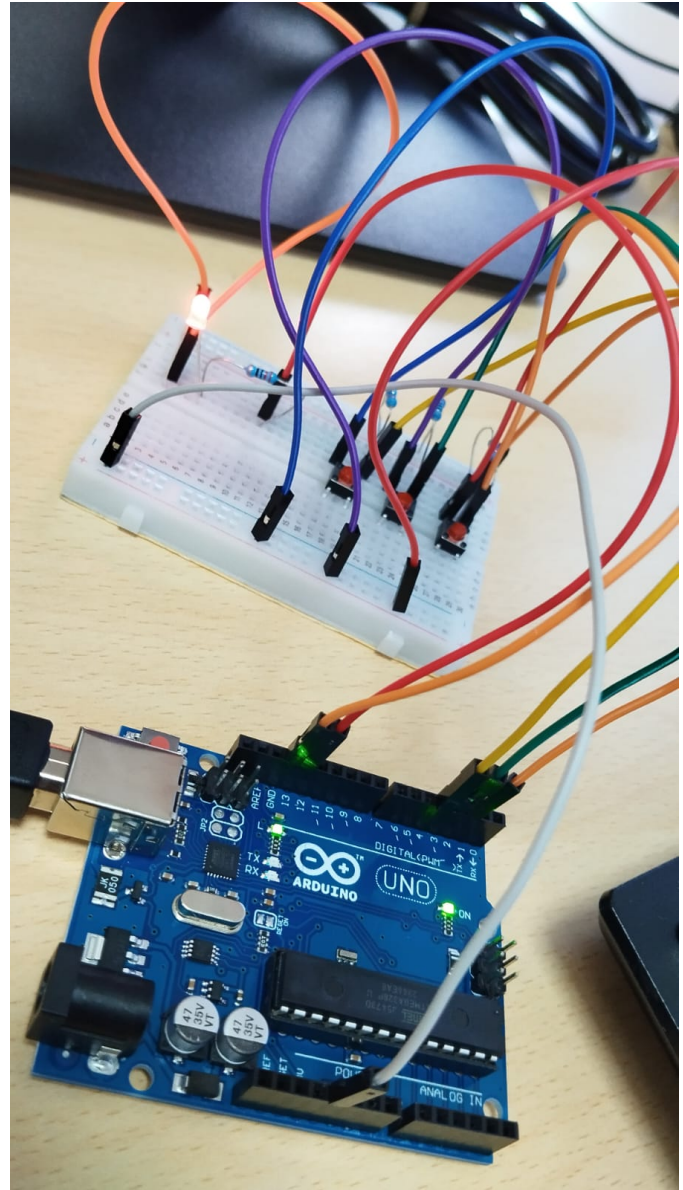GitHub Repo: github.com/aisusmitha/FWC.git



Experiment Setup (Representative)