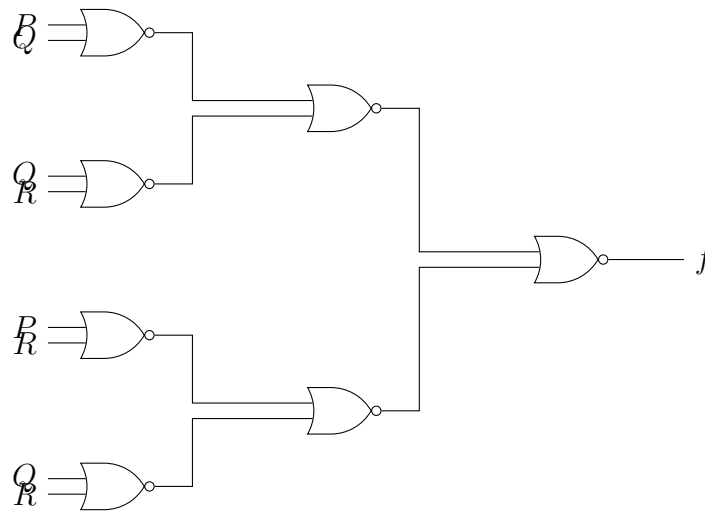


GATE QUESTION CSE 2010 Q31

Question

Q.31 What is the boolean expression for the output f of the combinational logic circuit of NOR gates given below?



(A) $\overline{Q + R}$

(B) $\overline{P + \overline{Q}}$

(C) $\overline{P + R}$

(D) $\overline{P + Q + R}$

Solution:

We are given a logic circuit made entirely of NOR gates, and we are to determine the Boolean expression for the output f .

Recall: A NOR gate performs the operation:

$$A \downarrow B = \overline{A + B}$$

Step-by-step Analysis

- Let the intermediate outputs of the NOR gates be labeled as follows:

$$A = \overline{P + Q}$$

$$B = \overline{Q + R}$$

$$C = \overline{P + R}$$

$$D = \overline{Q + R}$$

2. The next layer of NOR gates takes inputs as follows:

$$E = \overline{A + B} = \overline{\overline{P + Q} + \overline{Q + R}}$$
$$F = \overline{C + D} = \overline{\overline{P + R} + \overline{Q + R}}$$

3. The final output is:

$$f = \overline{E + F} = \overline{\overline{\overline{P + Q} + \overline{Q + R}} + \overline{\overline{P + R} + \overline{Q + R}}}$$

4. On simplifying or testing the expression through truth tables, we find that the output is high only when both $Q = 0$ and $R = 0$. This corresponds to:

$$f = \overline{Q + R}$$

Final Answer:

$$\boxed{f = \overline{Q + R}} \quad (\text{Option A})$$